

1.4 DATA TYPES & STRUCTURES · 1.4.3

Adders & D-type flip-flops

Original practice questions · 30 marks · about 40 minutes · spec 1.4.3(e)

Instructions. Answer all questions. Marks are shown in brackets []. Notation: $\cdot$ = AND, $+$ = OR, $\oplus$ = XOR.

1**Total: 6 marks**

A half adder adds two binary digits A and B, producing a sum S and a carry C.

- (a) Write a Boolean expression for S in terms of A and B. _____ [1]
- (b) Write a Boolean expression for C in terms of A and B. _____ [1]
- (c) Draw a logic gate diagram for the half adder. [2]



- (d) Explain why it is called a *half* adder. _____ [1]
- (e) When the half adder computes $1 + 1$, state the values of S and C. _____ [1]

2

Total: 6 marks

A full adder adds A, B and a carry-in (Cin).

(a) State the number of inputs a full adder has. _____ [1]

(b) Complete the truth table for the full adder. [4]

A	B	Cin	S	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

(c) Describe how full adders are used to add two multi-bit binary numbers. [1]

.....

3

Total: 6 marks

(a) State the purpose of a D-type flip-flop. [2]

.....

(b) Name the inputs and the outputs of a D-type flip-flop. [2]

.....

(c) Describe how a D-type flip-flop stores a bit, referring to the clock. [2]

.....

4

Total: 6 marks

- (a) Write the Boolean expression for the sum S of a full adder, in terms of A , B and C_{in} . [1]

- (b) Write the Boolean expression for the carry-out C_{out} of a full adder. [2]
- (c) State what flip-flops are used to build. _____ [1]
- (d) Explain the role of the clock when many flip-flops are used together. [2]

5

Total: 6 marks

- (a) For a full adder with $A = 1$, $B = 1$, $C_{in} = 1$, state the outputs S and C_{out} . [2]

- (b) Explain how these outputs correspond to the binary addition $1 + 1 + 1$. [2]

- (c) State how many full adders would be needed to add two 8-bit numbers. [1]

- (d) State the type of gate that produces the sum output in a half adder. _____ [1]

END OF QUESTIONS