


1.4 DATA TYPES & STRUCTURES · 1.4.3

Karnaugh maps — Mark scheme

38 marks · spec 1.4.3(b) · all groupings verified


AO key: AO1 = knowledge · AO2 = application. Shaded squares = the 1s. Every grouping checked programmatically. Map layout: cols CD 00·01·11·10, rows AB 00·01·11·10.

Q	ANSWER	AO	MARKS
1	(a) $\neg A \cdot \neg C$ — top-left block (b) $B \cdot D$ — centre block (c) $\neg B \cdot \neg D$ — four corners 2 marks each: correct 1s placed (1) + correct single ring of four (1). (6)	AO2	6
2(a)	Four 1s placed correctly (1); single group of four ringed (1); B is constant (=1) and D is constant (=1) across the group (1); simplified = $B \cdot D$ (1). (4)	AO2	4
2(b)	Four corner 1s placed (1); grouped as one block of four via wrap-around (1); B = 0 and D = 0 across the group (1); simplified = $\neg B \cdot \neg D$ (1). (4)	AO2	4

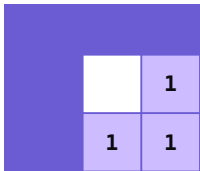Q	ANSWER	AO	MARKS
3	 Three 1s placed (all except A=0,B=0) (1); ring the whole bottom row (A=1) → gives A (1); ring the right column (B=1) → gives B (1); result $A + B$, proving the identity (1). (4)	AO2	4

Q	ANSWER	AO	MARKS
4(a)	Two groups of four. (1)	AO2	1
4(b)	Centre block = $B \cdot D$ (1); four corners = $\neg B \cdot \neg D$ (1); expression = $B \cdot D + \neg B \cdot \neg D$ (1). (This is XNOR of B and D.) (3)	AO2	3
4(c)	The map wraps around: the left and right edges are adjacent, and the top and bottom edges are adjacent (1); so the four corners differ in only one variable from their neighbours and form a valid group of four (1). (2)	AO1	2

Q	ANSWER	AO	MARKS
5	(i) 1 (1); (ii) 2 (1); (iii) 4 (1); (iv) 8 (1). (Each missing variable doubles the number of squares.) (4)	AO2	4

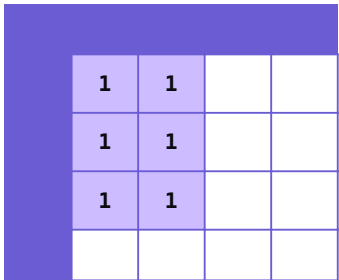Q	ANSWER	AO	MARKS
6(a)	 Six 1s placed correctly (1); group $\neg A \cdot \neg C$ = top-left four (rows 00, 01) (1); overlapping group $B \cdot \neg C$ = rows 01, 11 in the left two columns (1). (3)	AO2	3
6(b)	$\neg A \cdot \neg C + B \cdot \neg C$ (2) (1 mark per correct term). Accept the further-factorised $\neg C \cdot (\neg A + B)$.	AO2	2
6(c)	Two 2-input AND gates + one OR gate, plus inverters for $\neg A$ and $\neg C$ — accept "3 main gates (2 AND, 1 OR) plus NOT gates", or 1 AND + 1 OR + NOTs if the factorised form $\neg C \cdot (\neg A + B)$ is used. (1)	AO2	1

Q	ANSWER	AO	MARKS
7(a)	Grouping relies on combining adjacent cells that differ in one variable, which cancels that variable (1); this halving/doubling only works for rectangular blocks of 1, 2, 4, 8... (powers of two) (1). (2)	AO1	2
7(b)	A larger group means more variables are constant-or-cancelled, so each product term has fewer variables (1); fewer/smaller terms = fewer gates = the simplest circuit (1). (2)	AO1	2

Total for worksheet: 38 marks